

EMI Filter for Audio Equipment

By K5PA


March 5, 2014

Problem Statement

- During amateur radio transmission, our audio equipment would pick up the transmission, especially during CW operations
- Design and installation of simple Pi (C-L-C) network filters in the input of the stereo equipment solved the problem

Schematic (Need 2 Channels for Stereo)

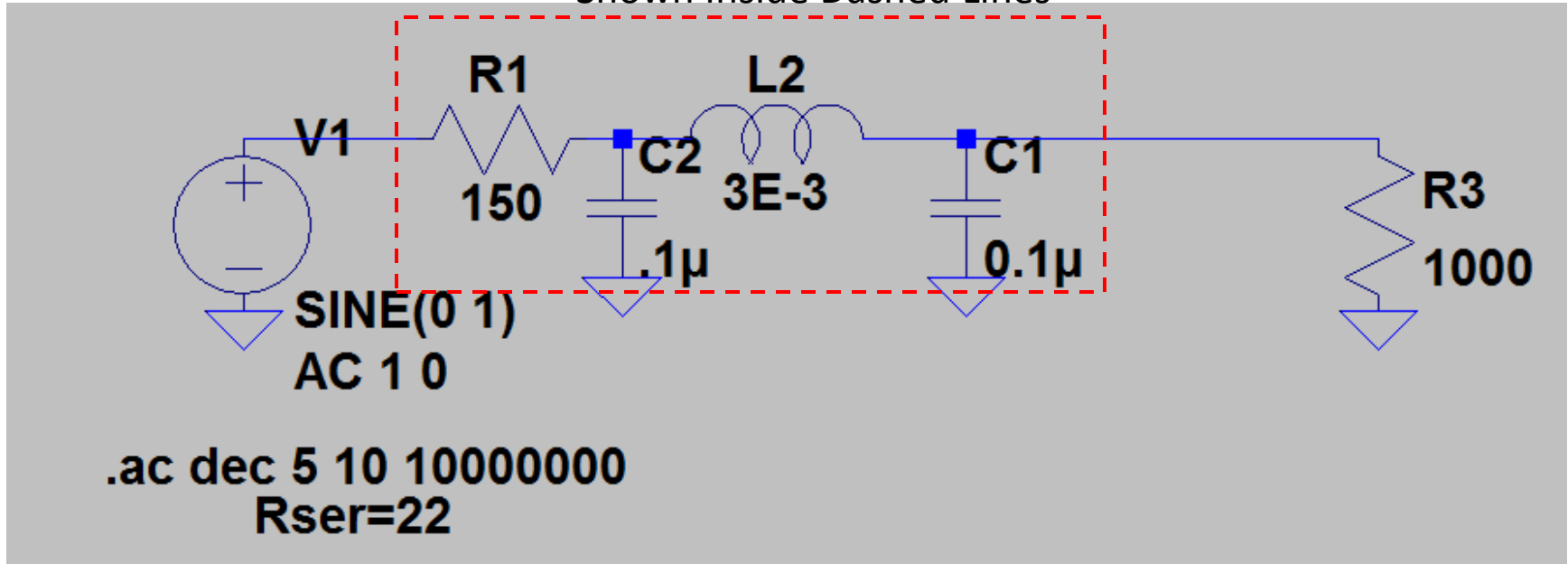Filter Circuit Board Components
Shown Inside Dashed Lines



SPICE Model Created Using Ltspice IV

L2 Uses Amidon Core, Type FB-73-2401,
 $A_L=2500$, 35 turns of magnet wire,
approximate inductance calculated is 3 mH



Formula for Calculating Inductance

$$N = 1000 \sqrt{\frac{\text{desired 'L' (mh)}}{A_L \text{ (mh/1000 turns)}}$$

$$L(\text{mh}) = \frac{A_L \times N^2}{1,000,000}$$

$$A_L \text{ (mh/1000 turns)} = \frac{1,000,000 \times \text{'L' (mh)}}{N^2}$$

N = number of turns


L = inductance (mh)

A_L = inductance index (mh)/1000 turns)

Ferrite Cores Used


Ferrite Core Characteristics and Source:

<http://www.amidoncorp.com/fb-73-2401/>

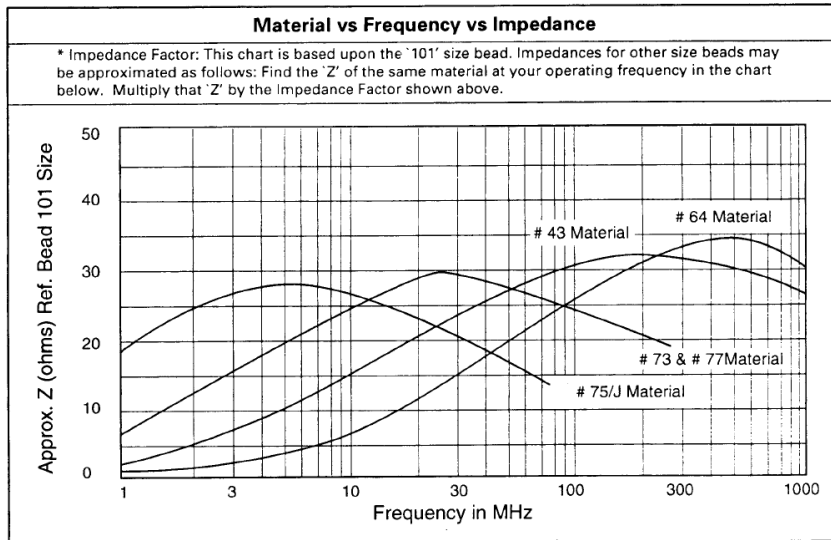

AMIDON INC. 240 Briggs Avenue, Costa Mesa, California 92626, U.S.A. • TEL. (714) 850-4660 • FAX (714) 850-1163

FB-73-2401

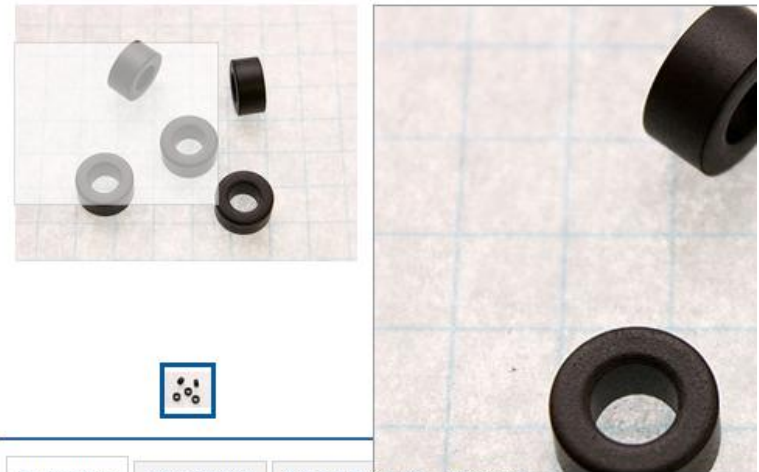


[Description](#) [Other Details](#) [Similar Products](#) [Reviews](#)

Product Description
Permeability 2500

ID: 0.197
OD: 0.380
Height: 0.190


Bode Plot of Pi Filter In/Out Response

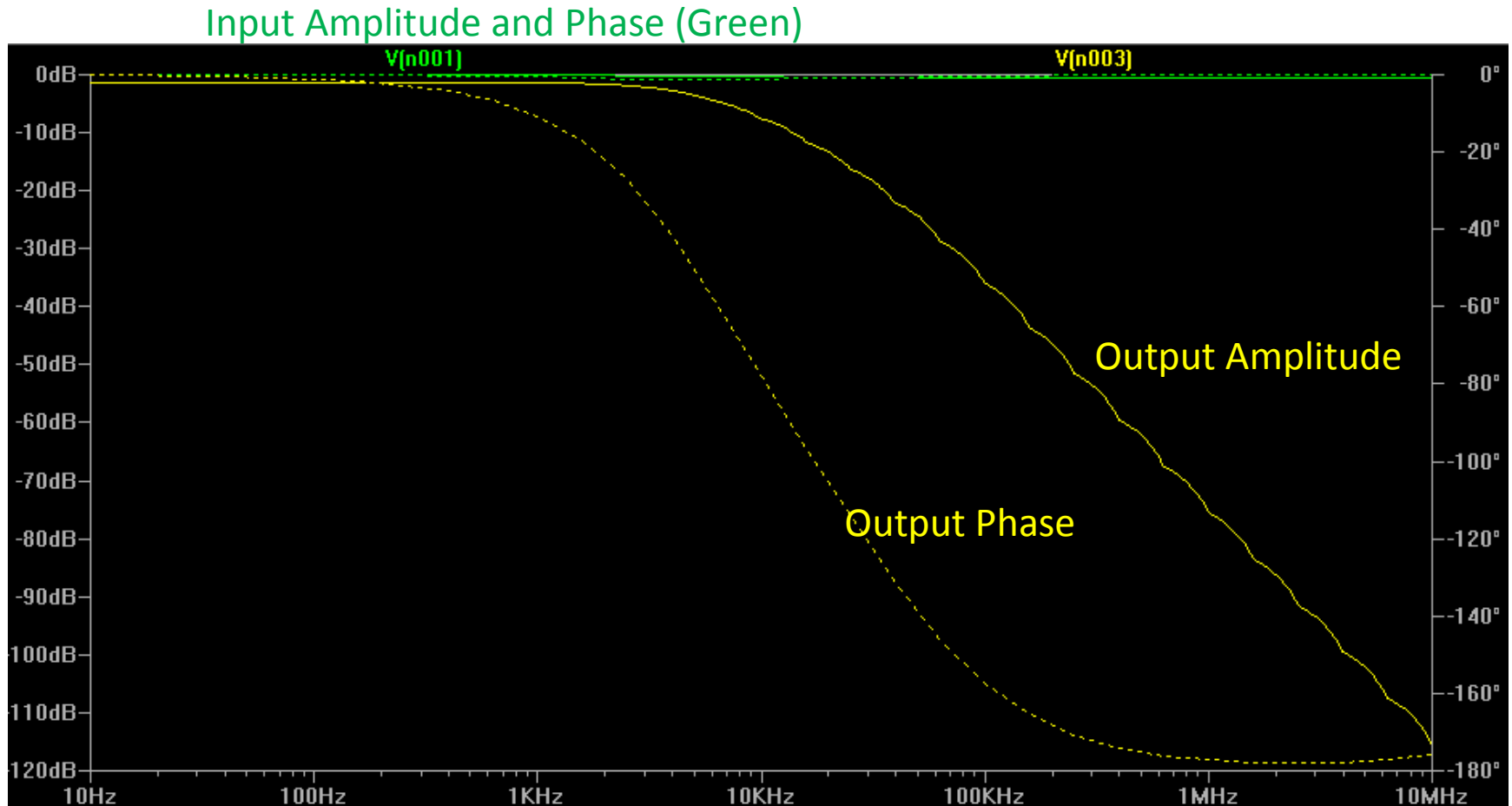

Subwoofer EMI Filter


- Same Pi Network Filter Used for Subwoofer

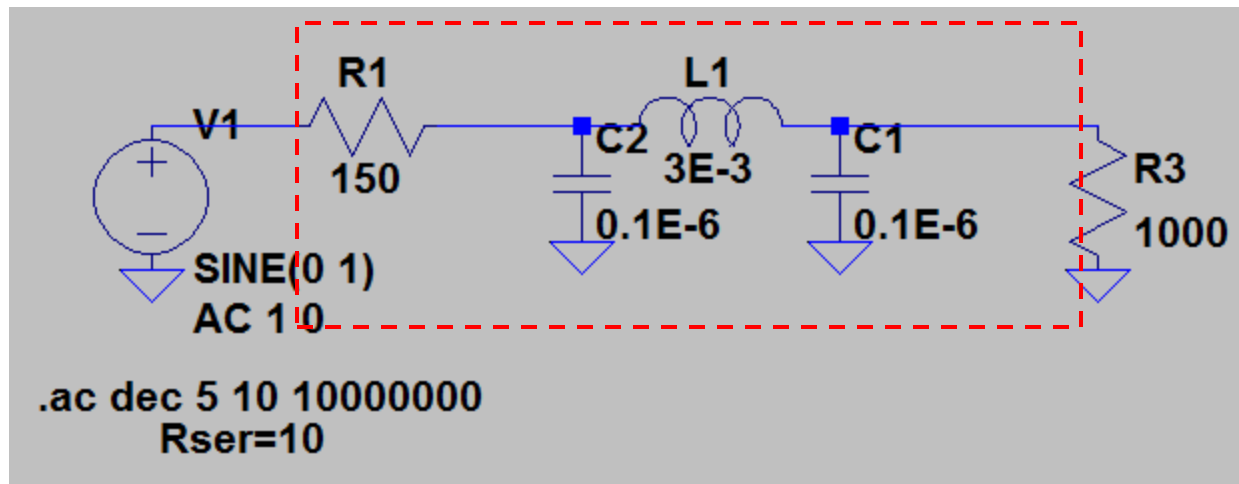Filter Circuit Board Components
Shown Inside Dashed Lines



Woofers Channel EMI Filter

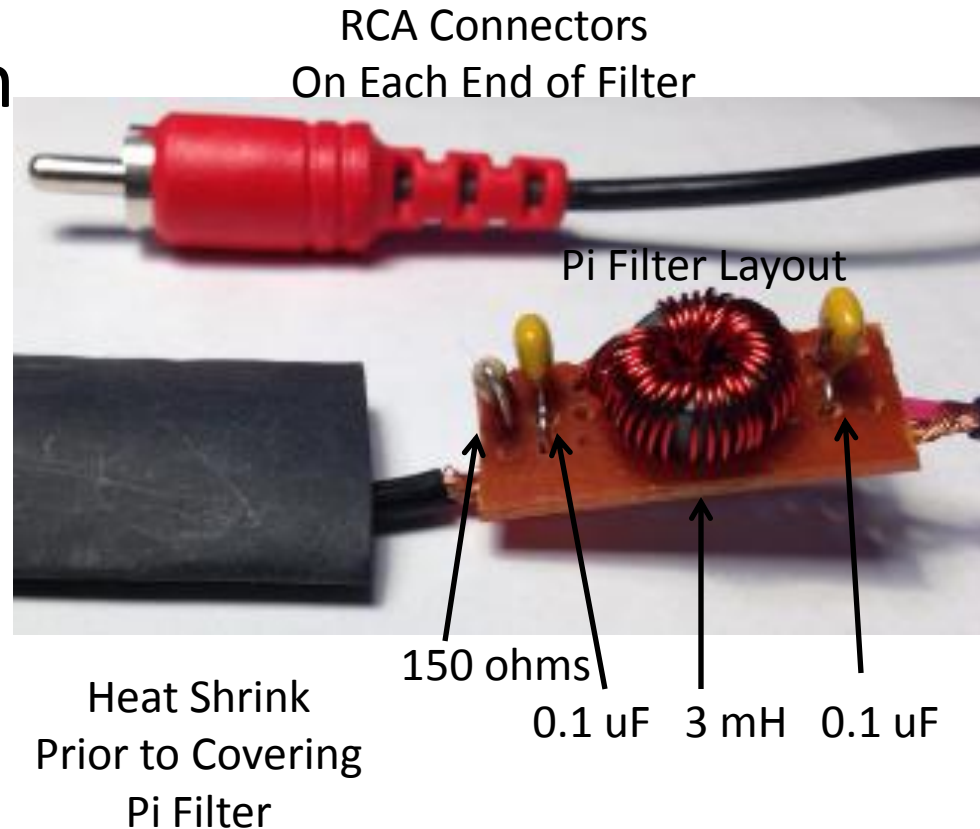- Filter EZ Construction Technique
- Cut One RCA to RCA Plug Cable in Half
- Insert Pi Filter with Heat Shrink Cover



Bode Plot of Pi Filter In/Out Response

